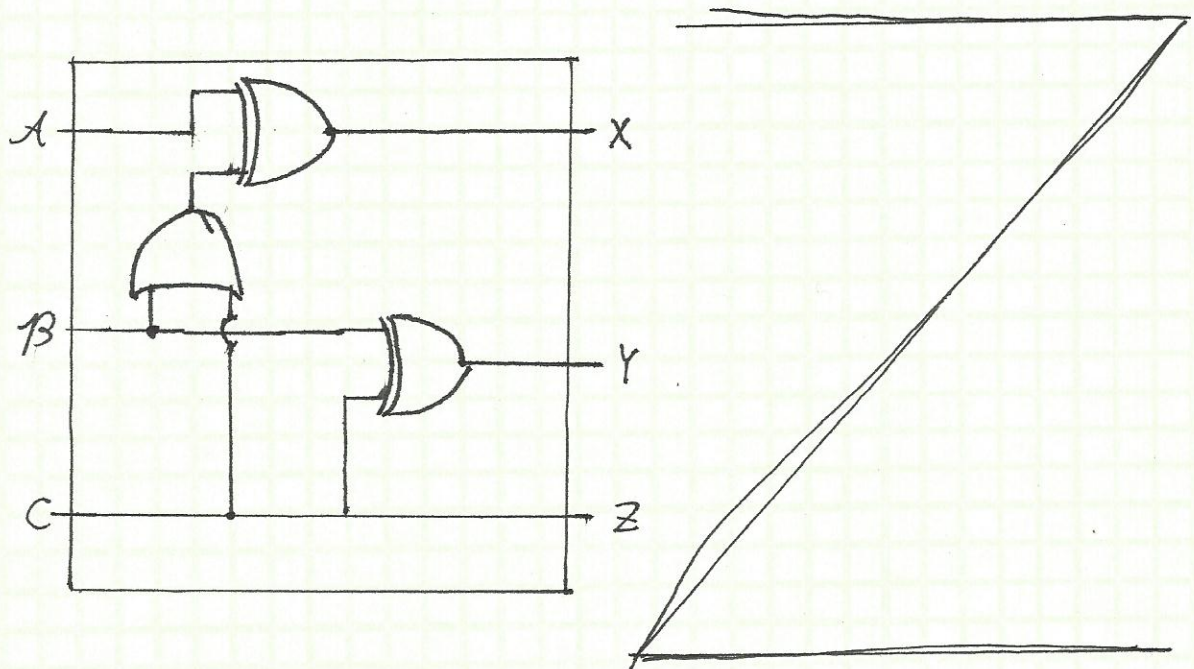
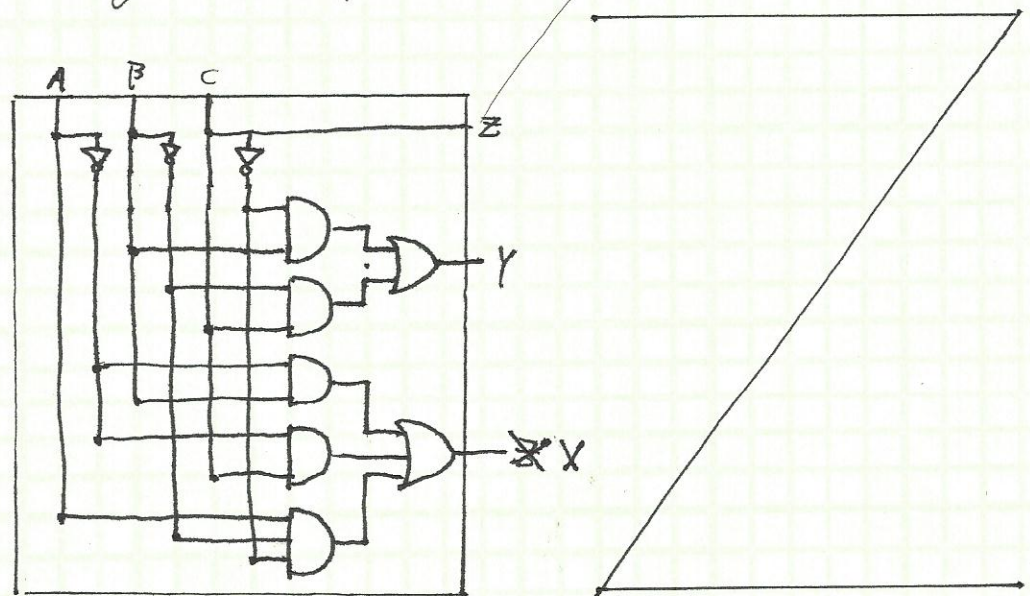


- 3- Draw circuits from Q-map equations
- Xor Gate implementation



- And & Not gate implementation



- Comparison: The first XOR Gate model has the advantage in simplicity and buildability. However the project may be constrained due to limited parts necessitating the more complex second design.